

# Computer Architecture (Lab). Week 12

Muhammad, Munir, Vladislav, Alena, Hamza, Manuel

Innopolis University

*m.fahim@innopolis.ru*

*m.makhmutov@innopolis.ru*

*v.ostankovich@innopolis.ru*

*a.yuryeva@innopolis.ru*

*h.salem@innopolis.university*


*m.rodriguez.osuna@innopolis.university*

November 19, 2020

# Topic of the Lab


- Delving further into a single-cycle processor
- Implementing simple ALU

# Single-Cycle Processor (1/2)

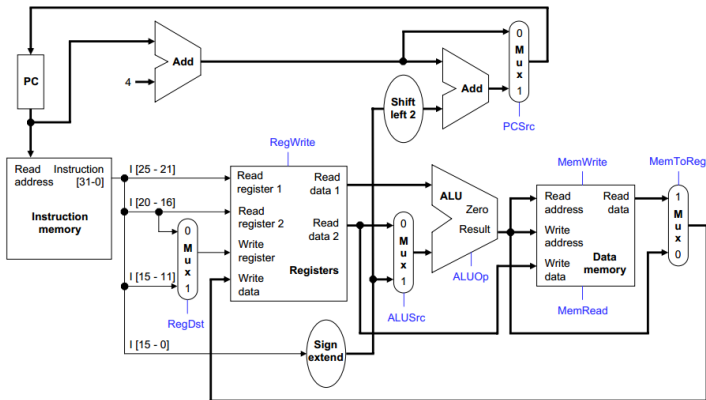

Overview of a single-cycle processor architecture. Can you explain the purpose of these blocks?

# Single-Cycle Processor (2/2)

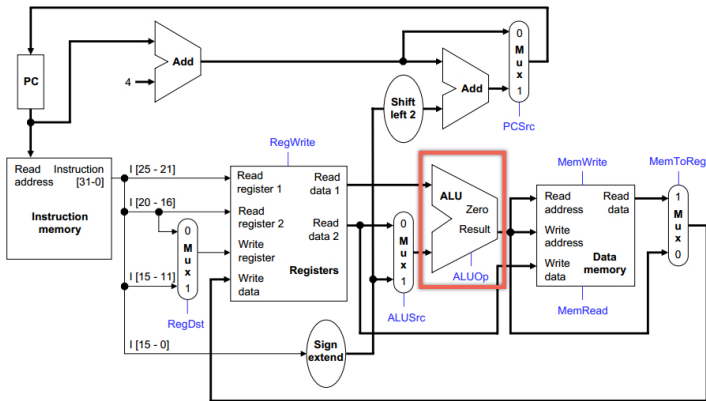

Focus on ALU for now. How can we implement MIPS compatible ALU in Verilog?

## ALU Operations (1/2)

In MIPS, ALU is accessed during execution of R-type operations

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

Opcode for ALU operations is 0x00. The meaning of an operation is specified by **funct** field. R-type operations include:

- add
- sub
- srl
- xor
- jr
- ...

## ALU Operations (2/2)

In MIPS, ALU is accessed during execution of R-type operations

op	rs	rt	rd	shamt	funct
6 bits	5 bits	5 bits	5 bits	5 bits	6 bits

ALU operations have the same **op**, but different **funct**:

- add \$rd,\$rs,\$rt

000000	xxxxxx	xxxxxx	xxxxxx	00000	100000
--------	--------	--------	--------	-------	--------

- sub \$rd,\$rs,\$rt

000000	xxxxxx	xxxxxx	xxxxxx	00000	100010
--------	--------	--------	--------	-------	--------

- srl \$rd,\$rt,3


000000	xxxxxx	xxxxxx	xxxxxx	00011	000010
--------	--------	--------	--------	-------	--------

## ALU Data Flow (1/2)

Suppose ALU that supports three operations: Addition, Subtraction, and Shift Right Logical. To build this ALU we need:

- Input data lines for the values of `$rs` and `$rt`
- Input line `funct` for choosing function type
- Input line for specifying `shamt` (Shift amount)
- Addition module
- Subtraction module
- Shift module
- Multiplexer that decides what goes to the output

## ALU Data Flow (2/2)

 

In the simplest implementation, all ALU functions are always calculated, but only one result is routed to the output.



# MUX implementation

MUX can be implemented using **case** operator in Verilog. Important properties of **case**:

- Assign operation can be performed only on wires
- case** can work only within **always@(...)** block

```
always@(*) begin
    case (register)
        value1: begin
            ...
        end
        value2: begin
            ...
        end
        default: begin
            ...
        end
    endcase
end
```

## Exercise

Implement an ALU that supports three operations: Addition, Subtraction, and Shift Right Logical. The inputs of the ALU are:

- `$rs` address (5-bit)
- `$rt` address (5-bit)
- `$rd` address (5-bit)
- `shamt` value (5-bit)
- `funct` value (6-bit)

Hint: Use `funct` codes from the slides above.

You are provided with a useful testbench module and expected output file.

## Exercise (cont.)

You need to implement following modules:

- **glob**: Module containing 32 32-bits MIPS registers. You should initialize array of 32 32-bits registers with zero values.
- **add**: Module for addition
- **sub**: Module for subtraction
- **srl**: Module for Shift Right Logical operation
- **mux**: Multiplexer module
- **alu**: ALU module

# Acknowledgements

- This lab was created and maintained by Vitaly Romanov, Aidar Gabdullin, Munir Makhmutov, Ruzilya Mirgalimova, Muhammad Fahim, Vladislav Ostankovich, Alena Yuryeva and Artem Burmyakov